

1 (a)

2 nA is obtained at 10°C
 $\times 2 \rightarrow 4 \text{ nA}$ " " " 20°C
 $\times 2 \rightarrow 8 \text{ nA}$ " " " 30°C
 $\times 2 \rightarrow 16 \text{ nA}$ " " " 40°C
 $\times 2 \rightarrow 32 \text{ nA}$ " " " 50°C

(b)

$T \uparrow$ $V_{ON} \uparrow$ $k_{\text{ate}} = 2.5 \text{ mV}/^\circ\text{C}$

(c)

i. p \rightarrow n direction \rightarrow forward biasing

$$I_D = I_S e^{\left(\frac{V_D}{nV_T}\right)}$$

$$\Rightarrow 5 \times 10^{-3} = 6 \times 10^{-9} e^{\frac{V_D}{0.0266}}$$

$$\Rightarrow V_D = 0.3626 \text{ V}$$

$$I_S = 6 \text{ nA}$$

$$n = 1$$

$$V_{ON} = 0.2 \text{ V}$$

$$V_{br} = -3 \text{ V}$$

[V_{br} is a -ve parameter]

$$T = 35^\circ\text{C}$$

$$= 308 \text{ K}$$

$$V_T = \frac{KT}{q} = 0.0266 \text{ V}$$

ii. $I_D = 0 \rightarrow$

we know, I_D becomes zero if

$$V_{app}/V_D \leq V_{ON}$$

$$\Rightarrow V_D \leq 0.2 \text{ V}$$

iii. $I_D = I_S = 6 \text{ nA}$ (n \rightarrow p) direction \rightarrow reverse biasing

$$-V_{br} < V_D < 0$$


$$\Rightarrow -3 < V_D < 0$$

21



Here,

$$V_{i, \text{RMS}} = \frac{V_{i, \text{max}}}{\sqrt{2}}$$
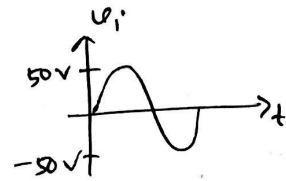
$$\Rightarrow V_{i, \text{max}} = 25\sqrt{2} \cdot \sqrt{2} = 50 \text{ V}$$



(a) for +ve h_c ,

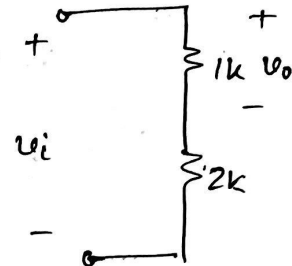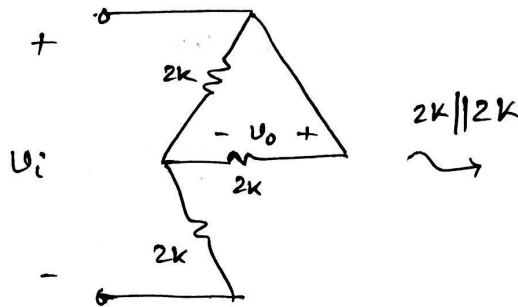


Voltage division rule,

$$v_o = \frac{1k}{1k + 2k} v_i$$



$$\Rightarrow v_o = \frac{v_i}{3}$$

for -ve h_c ,

$$v_o = -\frac{v_i}{3}$$

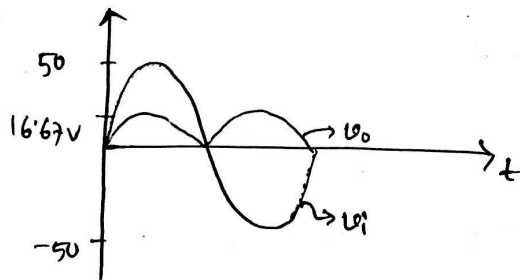

(b) for PIV, (-ve h_c)

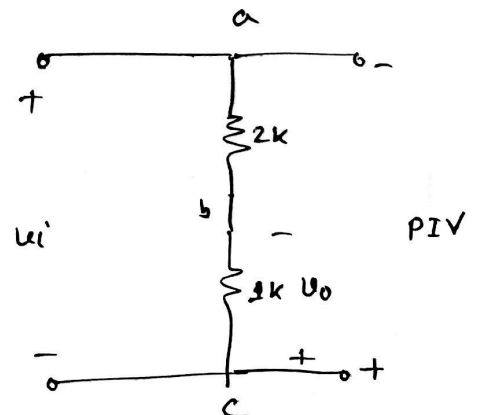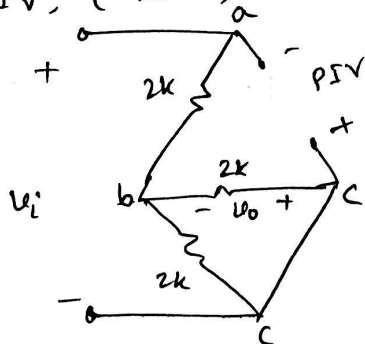

$$\text{PIV} = -v_i$$

$$= -v_{i, \text{max}} = -(-50)$$

$$= 50 \text{ V}$$


(c)

$V_i \rightarrow \text{sine wave} \rightarrow V_{i, \text{avg}} = 0$

$$\begin{aligned} V_o \rightarrow \text{full-wave} \rightarrow V_{o, \text{avg}} &= \frac{2}{\pi} \times V_{o, \text{max}} \\ &= \frac{2}{3.1416} \times 16.67 \\ &= 10.61 \text{ V} \end{aligned}$$

(e)

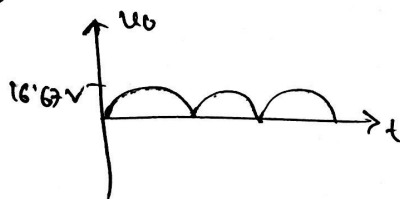(*) Only half wave rectifiers can be considered as clippers since $V_o = 0$ for in any half cycle of half-wave. Since the given circuit represents a full-wave,



V_o Can't be considered

(d)

$$|PIV| < |V_{br}|$$

$$\Rightarrow |V_{br}| > |PIV|$$

$$\Rightarrow |V_{br}| > 33.33 \text{ V}$$

91

for +ve V_i ,

$$V_o = -5 \text{ V} \rightarrow V_o \text{ is taken across diode}$$


for -ve V_i ,

$$V_o = V_i$$


↓

diode should be RBd

for -ve V_i

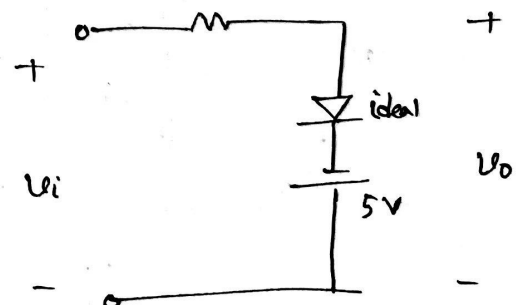

41

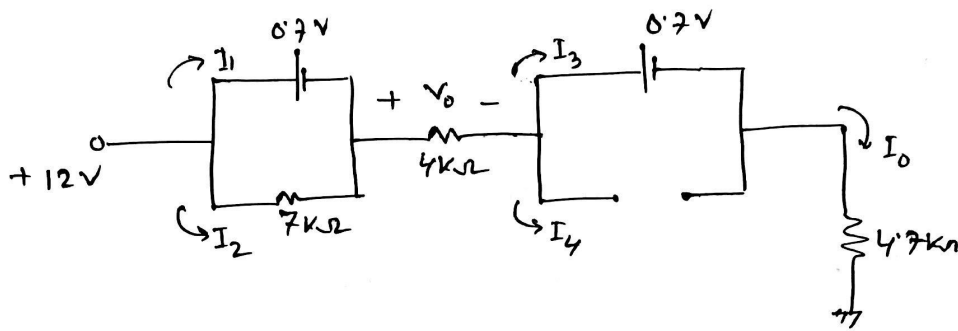

Here, $I_4 = 0$ & $I_3 = I_0$

KVL,

$$-12 + 0.7 + 4I_0 + 0.7 + 4.7I_0 = 0$$

$$\Rightarrow I_0 = 1.22 \text{ mA}$$

again, KVL,

$$-12 + 7I_2 + 4I_0 + 0.7 + 4.7I_0 = 0 \Rightarrow I_2 = 0.098 \text{ mA} \approx 0.1 \text{ mA}$$

OK,

$$I_2 = \frac{0.7}{7} = 0.1 \text{ mA}$$

So, $I_1 = I_0 - I_2 = 1.12 \text{ mA}$

Finally,

$$I_1 = 1.12 \text{ mA}$$


$$I_2 = 0.1 \text{ mA}$$

$$I_3 = 1.2 \text{ mA}$$

$$I_4 = 0$$

$$V_0 = 4I_0 = 4.88 \text{ V}$$

51 for +ve hc,

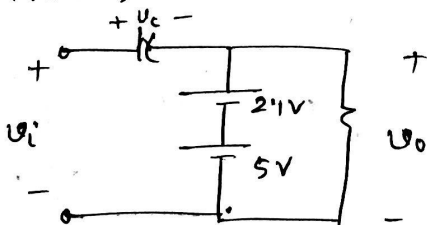


$$V_0 = 2.1 + 5$$

$$\Rightarrow V_0 = 7.1 \text{ V}$$

KVL,

$$V_i = V_c + V_0$$

$$\Rightarrow V_c = 7.9 \text{ V}$$

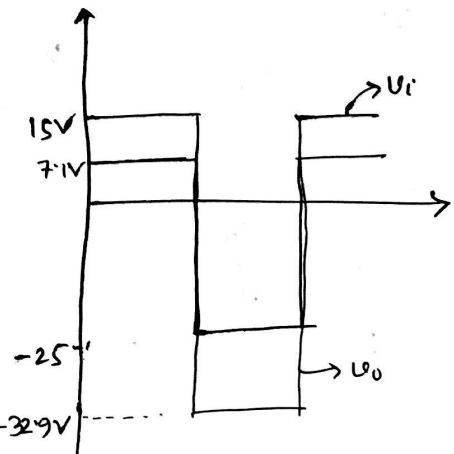

for -ve hc,

$$-V_i + V_c + V_0 = 0$$

$$\Rightarrow V_0 = V_i - V_c = -25 - 7.9$$

$$\Rightarrow V_0 = -32.9 \text{ V}$$

$$V_0 = \begin{cases} 7.1 \text{ V; +ve hc} \\ -32.9 \text{ V; -ve hc} \end{cases}$$